

Logic Gates

Truth - 1
False - 0


Binary

↳ 0, 1 digits

OR Gate (+)



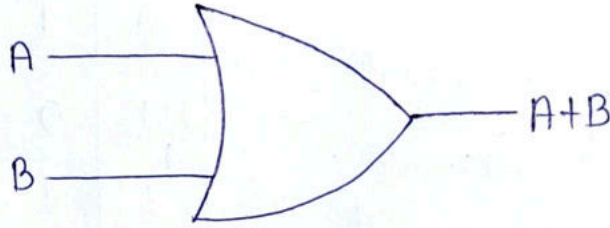
OR Gate gives you output as truth if one of the input is true



Truth table


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

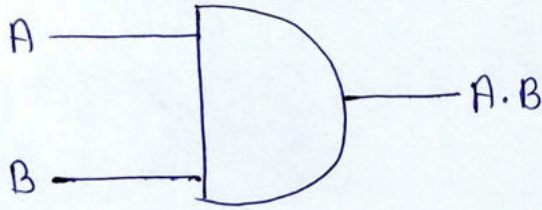AND GATE → AND Gate give truth as output if both the inputs are true.




A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

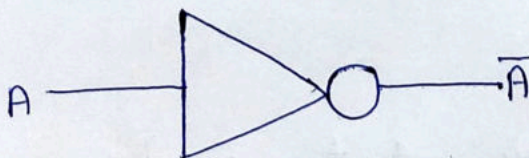NOT Gate (-) → NOT Gate gives output to the opposite of input



A	\bar{A}
0	1
1	0


NOR Gate \rightarrow (NOT + OR) Gate

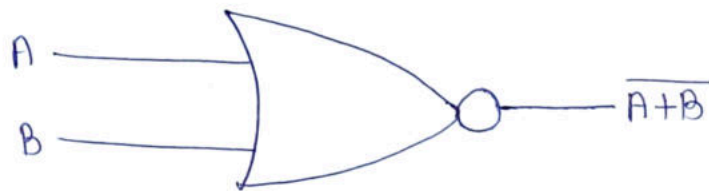


A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

\rightarrow the NOR Gate is a digital logic gate that implements logical NOR - a true result

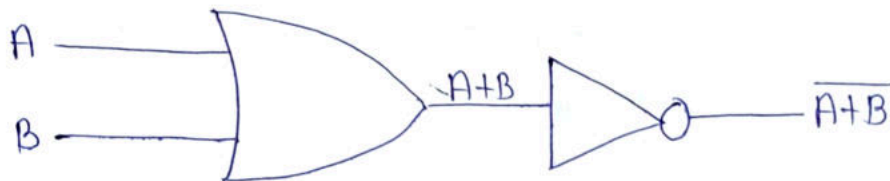(1) if both the inputs are false (0), otherwise output would be false.




NAND Gate \rightarrow (NOT + AND) Gate

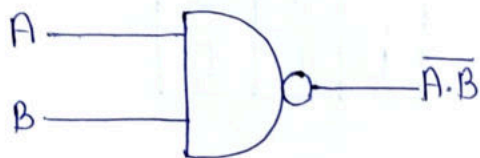


04

A	B	A.B	$\overline{A.B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

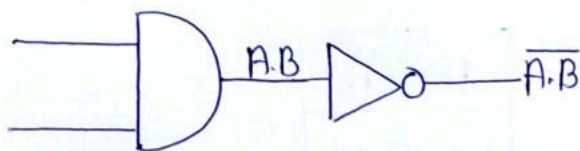

NAND Gate is ^{one} which gives you output as false only if both the inputs are true, otherwise output would be true

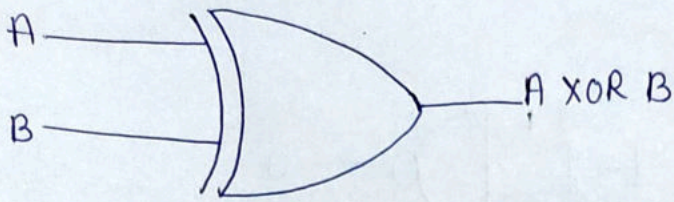XOR Gate \rightarrow (EXOR - Exclusive OR Gate)




A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0


XOR Gate gives you output as false when both inputs are same either '0' or '1', otherwise Input would be true

★ NOR Gate as universal gate

① NOR Gate as NOT

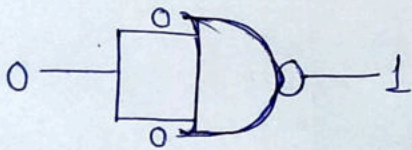


② NOR Gate as OR Gate

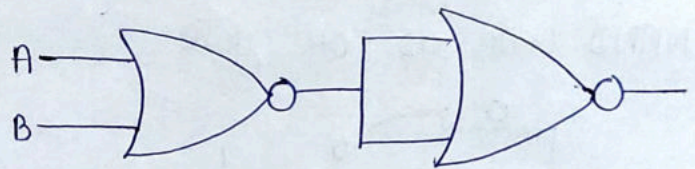

A	B	A+B
0	1	0
1	0	1

③ NOR Gate as AND Gate


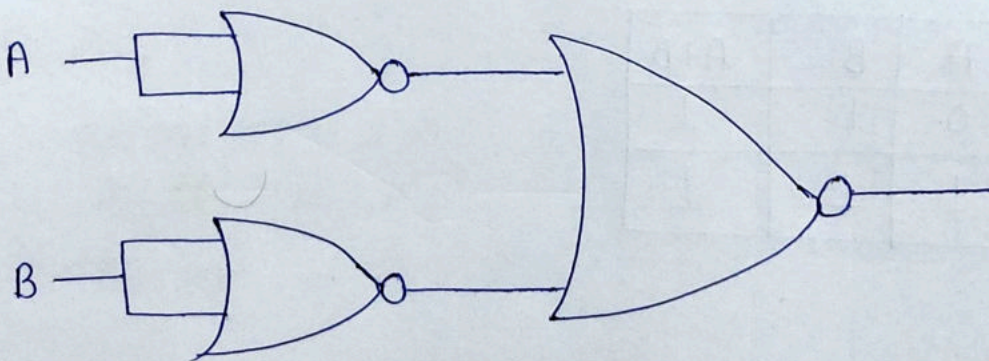


A	B	A.B
0	0	1
0	1	0
1	0	0
1	1	1



3

★ NAND Gate as universal gate


① NAND Gate as NOT Gate

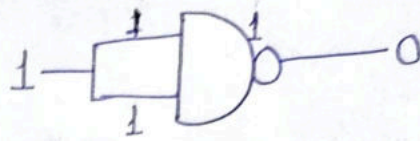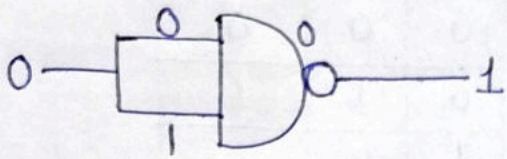

② NAND Gate as AND gate

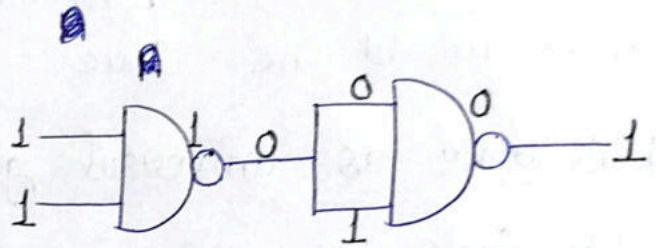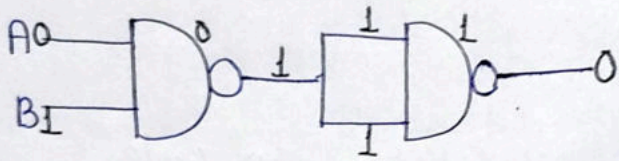

③ NAND Gate as OR gate

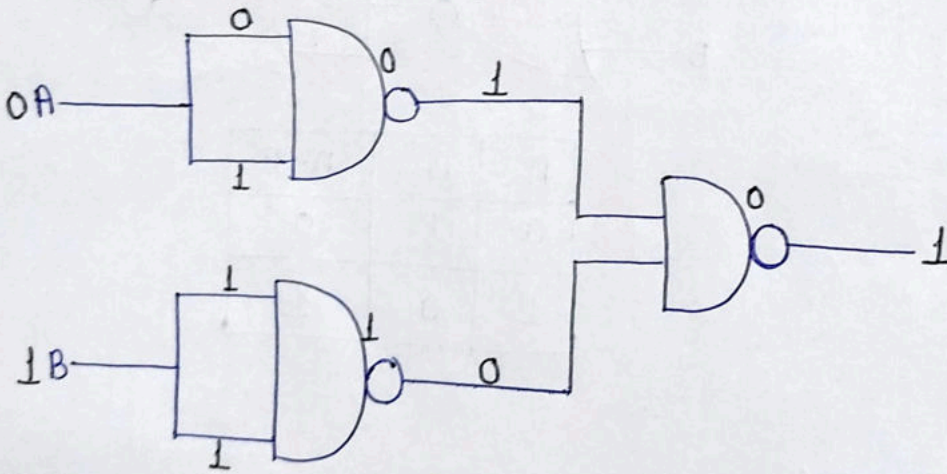

A	B	A+B
0	1	1
1	1	1

Boolean Algebra

Addition :

Addition	Result	Carry
0 + 0	0	0
0 + 1	1	0
1 + 0	1	0
1 + 1	0	1

Exo $11 + 3 = 14$

2	11	
2	5	1
2	2	1
	1	0

2	3	
	1	1

0	0
1	0
	1
	1
1	1
1	0

$$\begin{aligned} \Rightarrow & 1 \ 1 \ 1 \ 0 \\ & \quad 2^3 \ 2^2 \ 2^1 \ 2^0 \\ & = 2^3 \times 1 + 2^2 \times 1 + 2^1 \times 1 + 0 \\ & = 8 + 4 + 2 \\ & = 14 \end{aligned}$$

Exo $56 + 17 = ?$

Subtraction :

subtraction	-	0-0	0-1	1-0	1-1
Result	-	0	1	0	0
Borrow	-	0	1	0	0

Exo $26 - 14 = ?$

Soln:

2	26	
2	13	0
2	6	1
2	3	0
	1	1

2	14	
2	7	0
2	3	1
	1	1

0	0
1	0
	1
	1
0	1
0	1
0	0

$$\begin{bmatrix} 1 & 1 & 0 & 0 \\ 2^3 & 2^2 & 2^1 & 2^0 \\ 8+4 = 12 \end{bmatrix}$$

Multiplication :

multiplication -	0x0	0x1	1x0	1x1
Result -	0	0	0	1

Exo $101 \times 111 = ?$

Solⁿ:

$$\begin{array}{r} 101 \\ \times 111 \\ \hline 101 \\ 1010 \\ + 10100 \\ \hline 100011 \end{array}$$

Ans

Exo $12 \times 7 = ?$

Exo $14 \times 11 = ?$

Binary Division :

Exo

$$\begin{array}{r} 011 \\ 11 \overline{) 1011} \\ \underline{-11} \\ 011 \\ \underline{-11} \\ 0101 \\ \underline{-11} \\ 10 \end{array}$$

Exo

$$\begin{array}{r} 011 \\ 11 \overline{) 1001} \\ \underline{-11} \\ 0001 \\ \underline{-11} \\ 011 \\ \underline{-11} \\ 00 \end{array}$$

Basic identities of Boolean Algebra :

① $x+0 = x$

② $x+1 = 1$

③ $x+x = x$

④ $x \cdot 1 = x$

⑤ $x \cdot 0 = 0$

⑥ $x \cdot x = x$

⑦ $x + \bar{x} = 1$

⑧ $x \cdot \bar{x} = 0$

⑨ $\overline{(\bar{x})} = x$

Basic Laws:

Commutativity - (10) $x + y = y + x$

(11) $x \cdot y = y \cdot x$

Associativity - (12) $(x + y) + z = x + (y + z)$

(13) $(x \cdot y) \cdot z = x \cdot (y \cdot z)$

Distributive - (14) $x \cdot (y + z) = x \cdot y + x \cdot z$

(15) $x + (y \cdot z) = (x + y) \cdot (x + z)$

Exo Simplify - $F(x, y, z) = \bar{x}yz + \bar{x}y\bar{z} + xz$

Solⁿ:

$$F(x, y, z) = \bar{x}yz + \bar{x}y\bar{z} + xz$$

$$= \bar{x}(yz + y\bar{z}) + xz \quad (\text{by distributive law})$$


$$= \bar{x}y(z + \bar{z}) + xz \quad (\text{by distributive law})$$

$$= \bar{x}y \cdot 1 + xz \quad (\text{identity; } x + \bar{x} = 1)$$

$$F(x, y, z) = \bar{x}y + xz \quad \underline{\text{Ans}}$$

De-Morgan's Theorem - 1

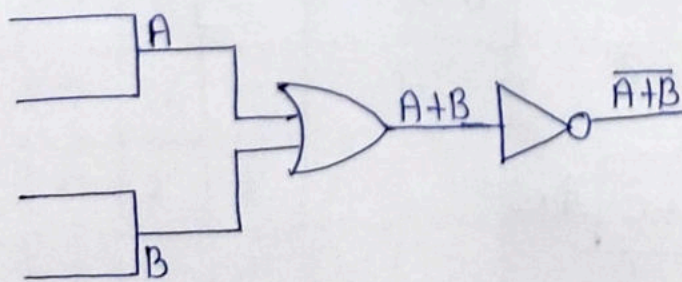
$$\overline{A+B} = \bar{A} \cdot \bar{B}$$



A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0


De-Morgan's Th. 2
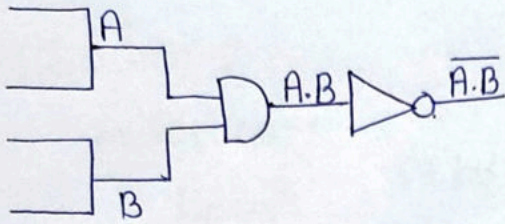
$$\overline{A \cdot B} = \bar{A} + \bar{B}$$




A	B	AB	$\overline{A \cdot B}$	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

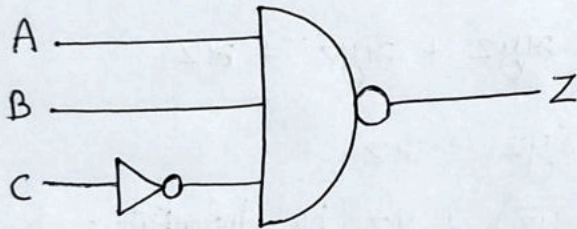Exo Determine the output expression for below circuit & simplify the output using De-Morgan's tho.



Solⁿ:

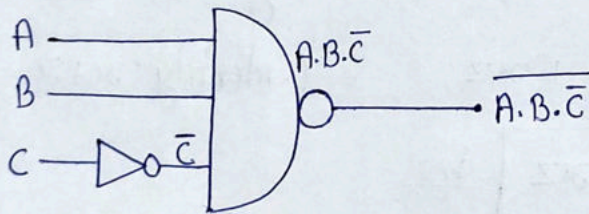

$$F(A, B, C) = \overline{A \cdot B \cdot \bar{C}}$$

Using de-morgan's tho, -

$$F(A, B, C) = \overline{A \cdot B \cdot \bar{C}}$$

$$F(A, B, C) = \bar{A} + \bar{B} + \bar{\bar{C}}$$

$$\boxed{\overline{A \cdot B} = \bar{A} + \bar{B}}$$

$$\boxed{F(A, B, C) = \bar{A} + \bar{B} + C} \text{ Ans}$$

Exo Write the boolean algebra expression $z(y+z)(x+y+z)$ in the simplest form using boolean postulates. Verify your result by constructing truth table.

Soln,

$$\begin{aligned}
 F(x, y, z) &= z(y+z)(x+y+z) \\
 &= (zy + z \cdot z)(x+y+z) \quad (\text{By distributive law}) \\
 &= (zy + z)(x+y+z) \quad (\text{identity ; } x \cdot x = x) \\
 &= (zy + z) \cdot x + (zy + z) \cdot y + (zy + z) \cdot z \quad (\text{distributive law}) \\
 &= zy x + z x + zy \cdot y + zy + \overline{z} y z + z z \\
 &= x y z + x z + \underline{y z} + \underline{y z} + y z + z \quad \left[\begin{array}{l} \text{commutative} \\ \text{identity ; } x \cdot x = x \end{array} \right] \\
 &= x y z + x z + \underline{y z} + \underline{y z} + z \quad (\text{identity ; } x + x = x)
 \end{aligned}$$

$$\boxed{F(x, y, z) = x y z + x z + y z + z} \quad (\text{identity ; } x + x = x)$$

Truth table

x	y	z	y+z	x+y+z	$z(y+z)(x+y+z)$	$x y z$	$x z$	$y z$	$x y z + x z + y z + z$
0	0	0	0	0	0	0	0	0	0
0	0	1	1	1	1	0	0	0	1
0	1	0	1	1	0	0	0	0	0
0	1	1	1	1	1	0	0	1	1
1	0	0	0	1	0	0	0	0	0
1	0	1	1	1	1	0	1	0	1
1	1	0	1	1	0	0	0	0	0
1	1	1	1	1	1	1	1	1	1